



Registration No:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages :2

AR-19

B.TECH 1<sup>ST</sup> SEMESTER EXAMINATIONS (REGULAR), NOV/DEC 2019

BESBS1033 – Basics of Electronics

Time : 3 Hours

Maximum : 70 Marks

Answer ALL Questions

The figures in the right hand margin indicate marks.

PART – A: (Multiple Choice Questions) 10 × 1=10 Mark

Q.1. Answer All Questions.

- a The forward voltage drop across a silicon diode is about [CO 1][PO 1]  
a)2.5 V b)3 V c)10 V d) 0.7 V
- b The most widely used rectifier is [CO 1][PO 1]  
a) half-wave rectifier b) centre-tap full-wave rectifier  
c) bridge full-wave rectifier d)none of the above
- c The number of depletion layers in a transistor is [CO 1][PO 2]  
a)four b)three c)one d)two
- d The power gain in a transistor connected in which arrangement is the highest [CO 2][PO 2]  
a)common emitter b)common base c)common collector d)none of the above
- e If the reverse bias on the gate of a JFET is increased, then width of the conducting channel. [CO 2][PO 1]  
a) is decreased b)is increased c)remains the same d)none of the above
- f For an Op-amp with negative feedback, the output is [CO 2][PO 1]  
a)equal to the input b)increased  
c) fed back to the inverting input d)fed back to the noninverting input
- g The input stage of an Op-amp is usually a [CO 3][PO 1]  
a) differential amplifier b)class B push-pull amplifier  
c)CE amplifier d)swamped amplifier
- h The material used to coat inside the face of CRT is [CO 3][PO 1]  
a) Carbon b)Sulphur c)Silicon d)Phosphorous
- i Both OR and AND gates can have only two inputs. [CO 4][PO 1]  
a) True b) False
- j In 2's complement representation the number 11100101 represents the decimal number . [CO 4][PO 1]  
a) +37 b)-31 c)+27 d)-27

PART – B: (Short Answer Questions) 10x2=20 Marks

Q.2. Answer ALL questions

- a Explain the term doping and its need? [CO1] [PO1]
- b Why diodes are not operated in the breakdown region in rectifiers? [CO1] [PO1]
- c Discuss the need for biasing the transistor? [CO1] [PO1]
- d What is Op-Amp? [CO2] [PO2]
- e What is the use of horizontal and vertical amplifier in CRO? [CO2] [PO1]
- f How  $\alpha$  and  $\beta$  are related to each other? [CO2] [PO2]
- g Represent -27 in 2's complement form. [CO3] [PO1]
- h Why a two-input NAND gate is called universal gate? [CO3] [PO1]
- i What is meant by LED? What precautions are required to be observed in the use of LEDs? [CO4] [PO1]
- j What are the main purposes for which a common-collector amplifier may be used? [CO4] [PO1]

PART – C: (Long Answer Questions) 4x10=40 Marks



Answer ALL questions

Q.3

- |   |  |         |             |
|---|--|---------|-------------|
| a | Explain the working of PN junction diode under forward and reverse biased conditions?                                  | 5 Marks | [CO1] [PO1] |
| b | With the circuit diagram, explain the operation of center-tapped full wave rectifier? Draw input and output waveforms? | 5 Marks | [CO1] [PO1] |

OR

- |   |   |         |             |
|---|---|---------|-------------|
| c | Draw and explain the V-I characteristics of a silicon diode?  | 5 Marks | [CO1] [PO2] |
| d | Explain the operation of half wave rectifier and capacitor filter with a neat circuit diagram and waveform? | 5Marks  | [CO1] [PO1] |

Q.4

- |   |   |         |             |
|---|---|---------|-------------|
| a | Draw CE circuit and sketch the input and output characteristics also explain the operating regions by indicating them on the characteristics curve? | 6 Marks | [CO2] [PO2] |
| b | Explain the basic structure and operation of JFET with neat diagrams?   | 4 Marks | [CO2] [PO2] |

OR

- |   |  |         |             |
|---|--|---------|-------------|
| c | With a neat diagram explain input, output characteristics of a transistor in a CB configuration? | 5 Marks | [CO2] [PO1] |
| d | Explain the operation of an enhancement MOSFET with neat circuit diagram?                        | 5 Marks | [CO2] [PO4] |

Q.5

- |   |  |         |             |
|---|--|---------|-------------|
| a | Explain the block diagram of an operational amplifier?   | 5 Marks | [CO3] [PO1] |
| b | Explain the op-amp as a adder with neat circuit diagram? | 5Marks  | [CO3] [PO1] |

OR

- |   |  |         |             |
|---|--|---------|-------------|
| c | Explain the operation of an op-amp as a non-inverting amplifier with neat diagram and waveforms? | 6 Marks | [CO3] [PO2] |
| d | Define the following terms w.r.t op-amp?[4M]<br>(i) CMRR (ii) Slew-rate                          | 4Marks  | [CO3] [PO1] |

Q.6

- |   |                                      |        |             |
|---|--------------------------------------|--------|-------------|
| a | Realise Ex-OR using only NAND gates? | 4Marks | [CO4] [PO1] |
| b | State and prove De-Morgans theorems? | 6Marks | [CO4] [PO2] |

OR

- |   |  |         |             |
|---|--|---------|-------------|
| c | Realize Full adder circuit using NAND gates?   | 3 Marks | [CO4] [PO2] |
| d | Write the logical symbol, truth table and Boolean expressions of all the logic gates ( AND,OR,NOT,NOR,NAND ,EX-OR,EX-NOR)? | 7 Marks | [CO4] [PO1] |