



Registration No:

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

Total Number of Pages : 2

AR-19

B.TECH 1ST SEMESTER EXAMINATIONS (REGULAR), NOV/DEC 2019

BESBS1034 – Basic Electrical Engineering

Time : 3 Hours

Maximum : 70 Marks

Answer ALL Questions

The figures in the right hand margin indicate marks.

PART – A: (Multiple Choice Questions) 10 × 1=10 Mark

Q.1. Answer All Questions.

- a Ohm's law is not applicable to [CO1][PO1]
(a) DC circuits (b) High currents (c) Small resistors (d) Semi-conductors
- b Specific resistance of a substance is measured in [CO1][PO1]
(a) ohms (b) mhos (c) ohm-cm (d) cm/ohm
- c For solving parallel ac circuit, the method used is [CO2][PO1]
(a) Vector method (b) Admittance method (c) Symbolic or j – method (d) All of these
- d The net power in a series R-C circuit is [CO2][PO1]
(a) Zero (b) Positive (c) Negative (d) None of these
- e Which DC motor is generally preferred for cranes and hoists? [CO3][PO1]
(a) Series motor (b) Shunt motor
(c) Cumulatively compounded motor (d) Differentially compounded motor
- f The basic function of a transformer is to change [CO3][PO1]
(a) The level of the voltage (b) The power level
(c) The power factor (d) The frequency
- g In electrical measuring instruments electrical energy is converted to [CO3][PO1]
(a) Mechanical energy (b) Heat energy (c) Chemical energy (d) Light energy
- h Which triggering is the most reliable? [CO4][PO2]
(a) Forward voltage triggering (b) Gate triggering.
(c) dv/dt triggering. (d) Thermal triggering
- i Out of the following which one is not a unconventional source of energy? [CO4][PO2]
(a) Tidal power (b) Geothermal energy (c) Nuclear energy (d) Wind power
- j The efficiency of the power transformer is [CO4][PO2]
(a) 50% (b) 60% (c) 80% (d) 95%

PART- B: (Short Answer Questions) 10X2=20 Marks

Q.2. Answer All Questions


- a State the Kirchhoff's current law? [CO1][PO1]
- b List out the limitations of ohms law. [CO1][PO1]
- c Define the RMS value. [CO2][PO1]
- d Explain magnetic flux density? [CO2][PO1]
- e Classify the DC generators. [CO3][PO1]
- f List out the applications of synchronous motor? [CO3][PO1]
- g Classify the measuring instruments. [CO4][PO2]
- h Explain the fundamental concept of thyristor? [CO4][PO2]
- i Express the Synchronous speed and slip of Induction motor? [CO4][PO2]
- j Define function of a fuse? [CO4][PO2]

PART – C: (Long Answer Questions) 4×10=40 Marks

Answer ALL Questions

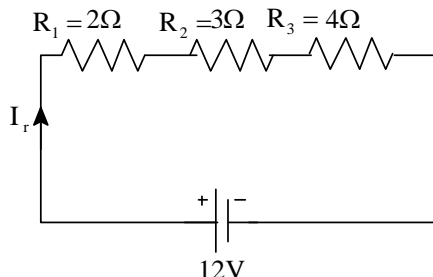
Q.3

- a Deduce the parallel connection of three resistors. 5M [CO1][PO1]
 b Find the currents and voltages across the resistances for the given network. 5M [CO1][PO1]




OR

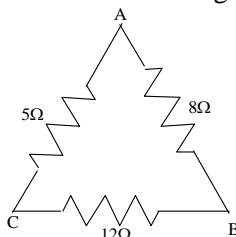- c Find the equivalent star connected circuit for the given delta connected circuit. 4M [CO1][PO1]



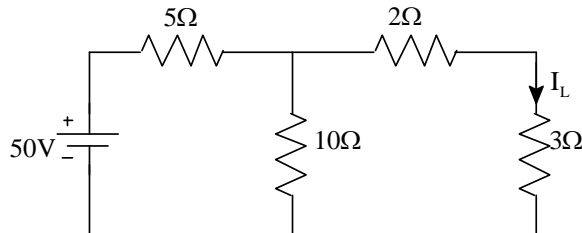- d Find the current through 3Ω resistance in the given circuit by using Thevenin's theorem. 6M [CO1][PO1]



Q.4

- a Deduce the sinusoidal excitation for RL series circuit. 7M [CO2][PO1]
 b Differentiate between single phase and three phase AC circuits. 3M [CO2][PO1]

OR

- c Discuss the hysteresis loss and eddy current loss. 4M [CO2][PO1]
 d An alternating voltage of RMS value 100V, 50Hz is applied separately across a resistance of 10Ω, an inductor of 100mH and a capacitor of 100μF. Calculate the current flow in each case and also draw and explain the Phasor diagrams. 6M [CO2][PO1]

Q.5

- a Discuss the working principle of DC generator. 5M [CO3][PO1]
 b Deduce the EMF equation of DC generator. 5M [CO3][PO1]

OR

- c Describe the working principle of transformer. 5M [CO3][PO1]
 d Deduce the EMF equation of transformer. 5M [CO3][PO1]

Q.6

- a Explain the working principle of PMMC instruments. 6M [CO4][PO2]
 b Differentiate between null type and deflecting type instruments. 4M [CO4][PO2]

OR

- c List the applications of Thyristor. 4M [CO4][PO2]
 d Demonstrate the various types of system of wiring. 6M [CO4][PO2]